

1) Calculate for the total resistance and total current through the circuit.

